

Feedback Circuits

P. Aashrith *

0.0.1. A dc amplifier having a single-pole response with pole frequency 10Hz and unity-gain frequency of 1MHz is operated in a loop whose frequency-independent feedback factor is 0.01. Find the low-frequency gain, the 3-dB frequency, and the unity-gain frequency of the closed-loop amplifier. By what factor does the pole shift?

Solution: The open-loop gain of the amplifier is

$$G(s) = \frac{A_o}{1 + \frac{s}{\omega_p}} = \frac{A_o}{1 + \frac{s}{2\pi \cdot 10}} \quad (0.0.1.1)$$

Given that unity gain frequency is 1MHz
Replacing s with $j\omega$ in this equation.

$$\left| \frac{A_o}{1 + \frac{j \cdot 2\pi \cdot 10^6}{2\pi \cdot 10}} \right| = 1 \quad (0.0.1.2)$$

$$|A_o| = \left| 1 + j \frac{2\pi \cdot 10^6}{2\pi \cdot 10} \right| \quad (0.0.1.3)$$

$$A_o \approx 10^5 \quad (0.0.1.4)$$

0.0.2. Draw the bode plots of open-loop circuit

Solution:

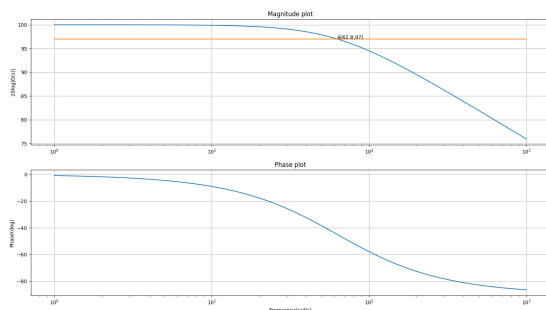


Fig. 0.0.2: Bode plots of Open-loop Transfer Function

Python code for above plot is

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India. All content in this manual is released under GNU GPL. Free and open source.

codes/ee18btech11035_bode1.py

0.0.3. Design a Circuit for $G(s)$

Solution: Designing $G(s)$ Using Op-amp with DC gain of 10^5 and a pole at 10Hz.

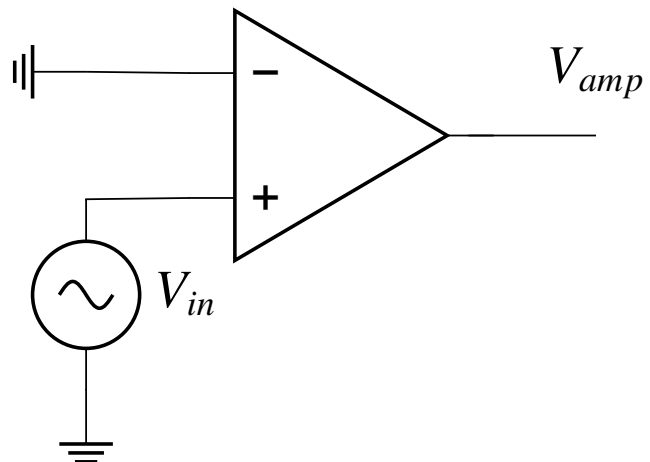


Fig. 0.0.3

0.0.4. Verify the gain using spice

Solution: Netlist file for simulation:

spice/ee18btech11035_spice1.net

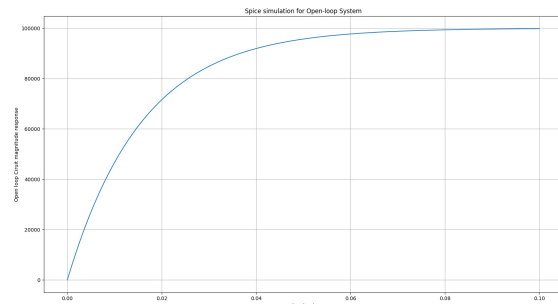


Fig. 0.0.4: Spice Simulation of Open-loop Transfer Function

Python code for above plot:

codes/ee18btech11035_spice1.py

0.0.5. Verification of step response of open-loop transfer function through python

Solution:

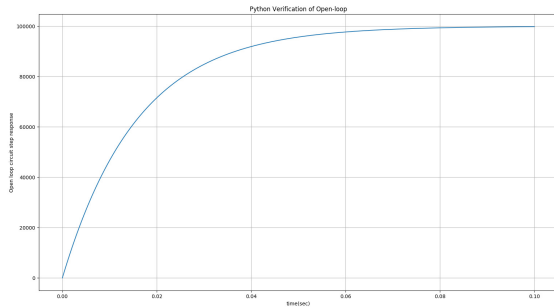


Fig. 0.0.5: Python verification of Open-loop Transfer Function

Python code for above verification is

```
codes/ee18btech11035_pythonverify1.py
```

0.0.6. Add a feedback for above circuit with a feedback factor of 0.01 and calculate closed-loop transfer function

Solution: $G(s) = \frac{10^5}{1 + \frac{s}{2\pi \cdot 10}}$ and $H(s) = 0.01$

$$T(s) = \frac{G(s)}{1 + G(s)H(s)} \quad (0.0.6.1)$$

$$T = \frac{\frac{A_O}{1 + A_O H(s)}}{1 + \frac{s}{20\pi(1 + A_O H(s))}} \quad (0.0.6.2)$$

$$T(s) = \frac{99.90}{1 + \frac{s}{2\pi \cdot 10010}} \quad (0.0.6.3)$$

Block diagram representation of the amplifier

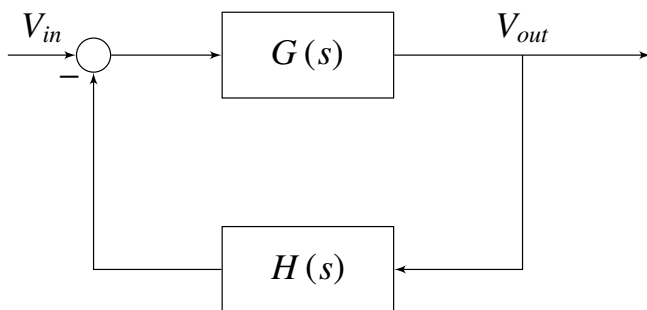


Fig. 0.0.6

0.0.7. Find the low frequency gain of the closed-loop amplifier.

Solution: As frequency is low, substituting

$$s = 0$$

$$T(0) = \frac{G(0)}{1 + G(0)H(0)} \quad (0.0.7.1)$$

$$= \frac{10^5}{1 + 10^5 \cdot (0.01)} \quad (0.0.7.2)$$

$$= 99.900 \quad (0.0.7.3)$$

0.0.8. Find the 3-dB frequency of the closed loop amplifier

Solution:

$$T = \frac{\frac{A_O}{1 + A_O H(s)}}{1 + \frac{s}{20\pi(1 + A_O H(s))}} \quad (0.0.8.1)$$

$$\text{3-dB frequency} = 20\pi \cdot (1 + A_O H(s)) \quad (0.0.8.2)$$

$$= 20\pi \cdot (1 + 10^5 \cdot (0.01)) \quad (0.0.8.3)$$

$$= 62862.8 \text{ rad/s} = 10.01 \text{ kHz} \quad (0.0.8.4)$$

0.0.9. Find the unity gain frequency of the closed loop amplifier

Solution: Unity-gain frequency of the closed loop amplifier is obtained as follows

$$|T| = 1 \quad (0.0.9.1)$$

$$\frac{A_O}{1 + A_O H(s)} = \left| 1 + \frac{j\omega}{20\pi(1 + A_O H(s))} \right| \quad (0.0.9.2)$$

$$99.900 = \left| 1 + \frac{j\omega}{62862.8} \right| \quad (0.0.9.3)$$

$$\omega = 6279.649 \text{ Krad/s} = 999.94 \text{ kHz} \quad (0.0.9.4)$$

0.0.10. By what factor does the pole shift?

Solution: Open-loop pole is 10Hz and the Closed-loop pole is $20\pi \cdot (1 + A_O H(s))$

$$\text{Pole-shift Factor} = \frac{20\pi(1 + A_O H(s))}{20\pi} \quad (0.0.10.1)$$

$$= 1 + A_O H(s) = 1001 \quad (0.0.10.2)$$

0.0.11. Design the feedback with $H(s) = 0.01$

Solution: Designing Feedback circuit:

As, Feedback is a constant value designing it by using simple voltage divider circuit

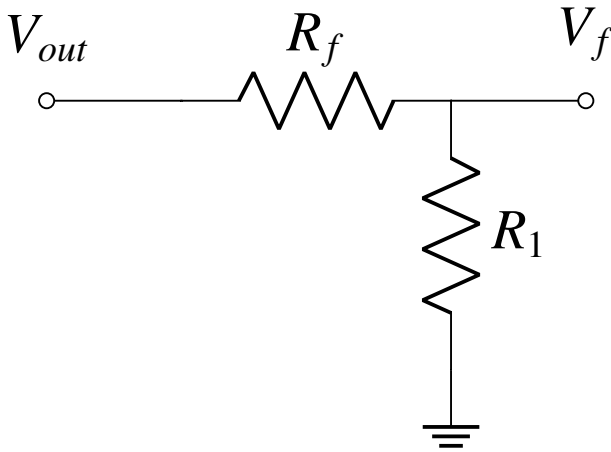


Fig. 0.0.11

$$\frac{V_f}{V_{out}} = \frac{R_1}{R_1 + R_f} = H(s) = 0.01 \quad (0.0.11.1)$$

Choosing R_1 as 10Ω and R_f as 990Ω

Overall Circuit is as follows:

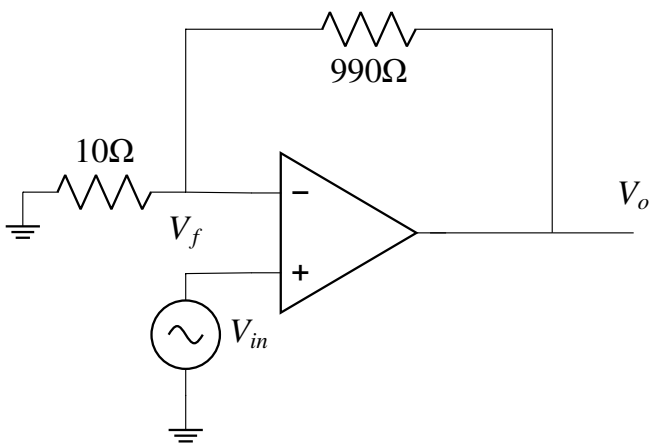


Fig. 0.0.11

Circuit Element	Parameter Value
Op-amp Gain	10^5
Op-amp pole	$10Hz$
R_1	10Ω
R_f	990Ω

TABLE 0.0.11

0.0.12. Draw the Bode plots of closed-loop circuit
Solution:

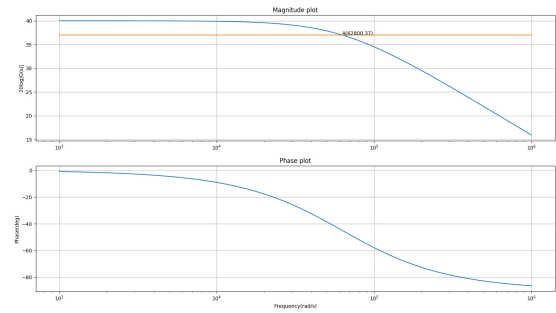


Fig. 0.0.12: Bode plots of Closed-loop Transfer Function

Python code for above plot is

codes/ee18btech11035_bode2.py

0.0.13. Verify the gain of closed loop Circuit using spice

Solution: Follow the Instructions for SPICE simulation:

spice/README.md

Netlist file for simulation:

spice/ee18btech11035_spice2.net

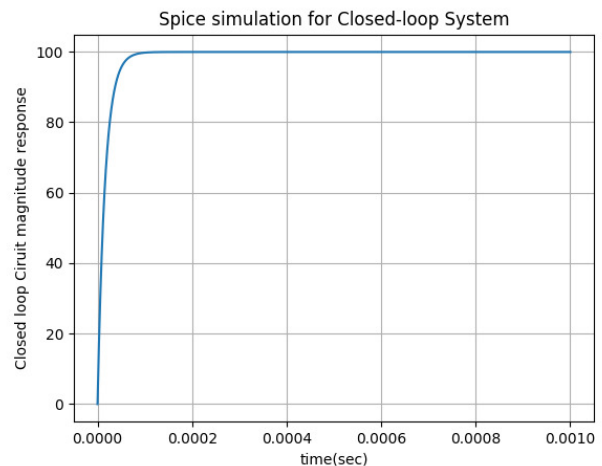


Fig. 0.0.13: Spice simulation of Closed-loop Transfer Function

Pyhton code for above plot:

codes/ee18btech11035_spice2.py

0.0.14. Verification of step response of open-loop transfer function through python
Solution:

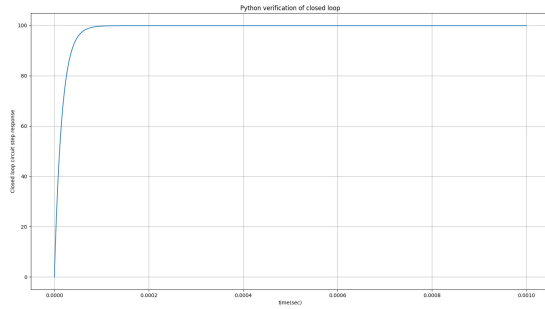


Fig. 0.0.14: Python verification of closed-loop Transfer Function

Python code for above verification is

codes/ee18btech11035_pythonverify2.py

0.0.15. Tabulating Gain Bandwidth and Gain bandwidth product

Solution:

	$G(s)$	$T(s)$
Gain	10^5	99.9
Band-width	20π	$20\pi.1001$
Gain band-width product	$2\pi.10^6$	$2\pi.10^6$

TABLE 0.0.15

Therefore, By using feedback we can get desired Gain of an amplifier while maintaining constant Gain Bandwidth product.